



Aim:

Given a 4-variable logic expression, simplify it using appropriate technique and realise the simplified logic expression using 8:1 multiplexer I.C.  
Hence,  $f(a, b, c, d) = \sum m(0, 1, 2, 4, 8, 9, 11, 15)$

APPARATUS:

trainer

- \* Digital IC ~~trainer~~ kit
- \* Patch cords
- \* IC-7404
- \* IC-74151

THEORY:

- \* Multiplexer is a logic circuit that switches digital data from several input lines on to a single output line in a specified time sequence.
- \* A mux has a several data input lines and a single output line. It also has data select inputs which permit digital data any one of the inputs to be switched to the output line.

Inputs				Output	
A	B	C	D	Y	$\bar{Y}$
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	0	1



\* it is of  $2^n$  multiplexer.  $2^n$  inputs to 1 output

\* An 8:1 mux has three select lines, whereas the given function is a 4-variable function

Result:

Realisation of Boolean expression using 8:1 mux is verified.