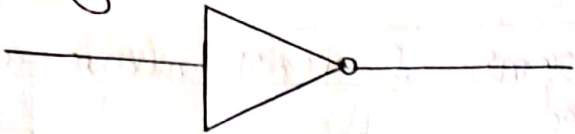


1. NOT Gate


Symbol




Truth table

I/p	O/p
0	1
1	0

Pin diagram GND

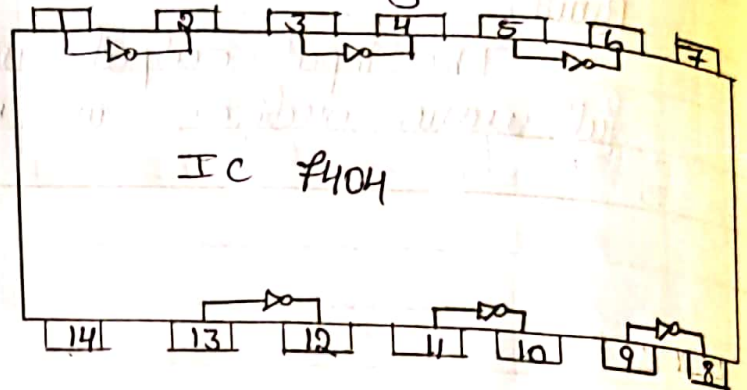


2. OR Gate

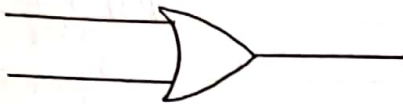

Truth table

A	B	O/p
0	0	0
0	1	1
1	0	1
1	1	1

Pin diagram GND

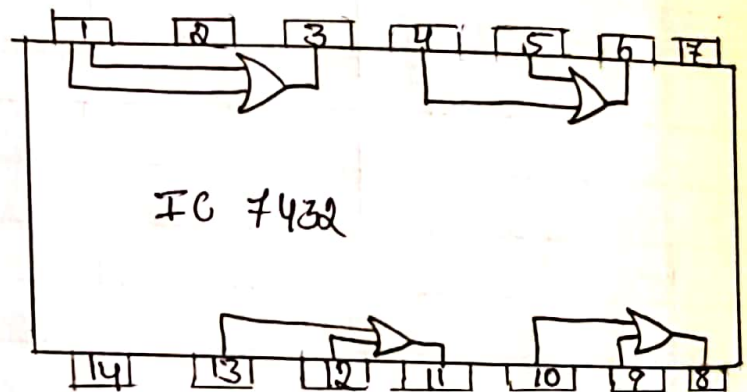

3. AND Gate


Symbol



Truth table

A	B	O/p
0	0	0
0	1	0
1	0	0
1	1	1

Pin diagram GND

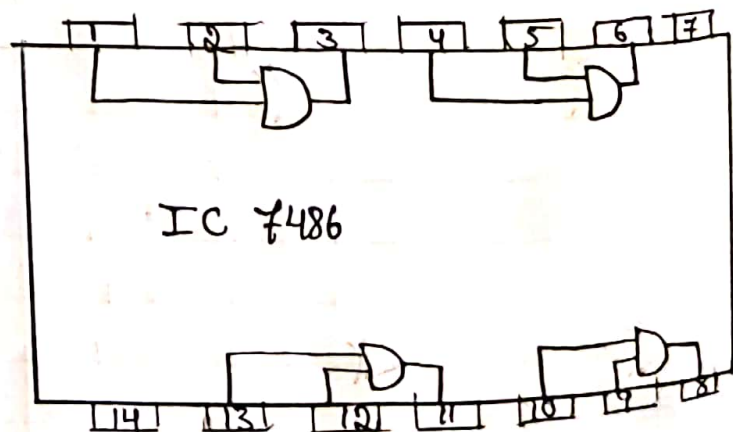

Name of the Experiment : i] Binary to Grey ii] ~~Grey~~ Grey to Binary

Aim:

Design and implement code converter

i] Binary to Grey

ii] Grey to Binary code

APPARATUS:

- * Digital IC ^{trainer} ~~trainer~~ kit
- * Patch cords
- * IC-7486


THEORY:

* There is a wide variety of binary code used in digital systems. Some of these are binary-coded decimal [BCD], Grey etc. it is required to convert from one code to another.

i] Binary code:

It is a straight binary code. The binary number system represents values using 2 symbols typically 0 and 1. computers call these bits as either off (0) and on (1) it is a weight code. Since a weight is assigned to every position


4. XOR Gate

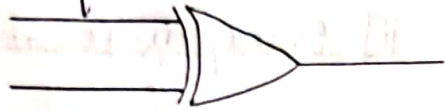

Truth table

A	B	O/P
0	0	0
0	1	0
1	0	0
1	1	1

Pin Diagram 7408

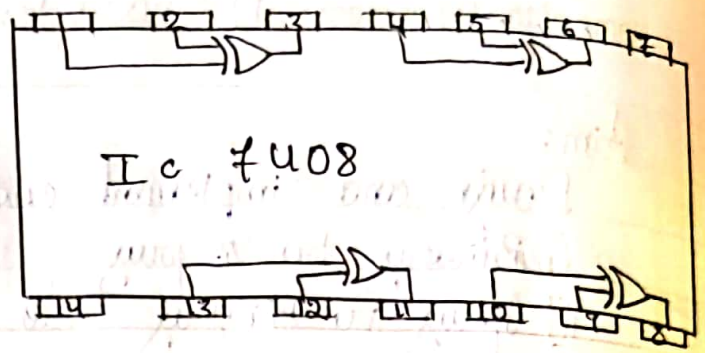

Binary to Grey


$(0101)_B \rightarrow$
MSB LSB

$$\therefore G_2 = B_2$$

$$G_1 = B_2 \oplus B_1$$

$$G_0 = B_1 \oplus B_0$$

circuit diagram.

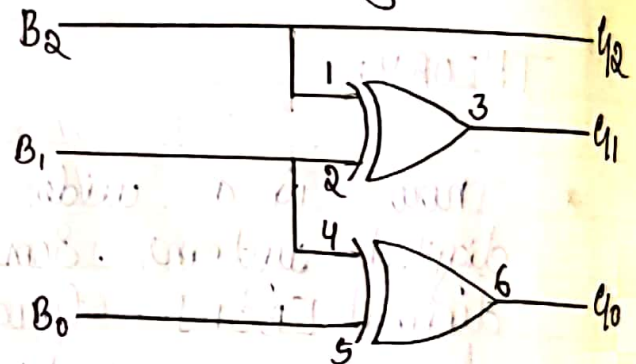

Truth table

Decimal equivalent	Binary code			Grey code		
	B_2	B_1	B_0	G_2	G_1	G_0
0	0	0	0	0	0	0
1	0	0	1	0	0	1
2	0	1	0	0	1	0
3	0	1	1	0	1	1
4	1	0	0	1	0	0
5	1	0	1	1	0	1
6	1	1	0	1	1	0
7	1	1	1	1	1	1

ii] Gray code:

It is a modified binary code in which a decimal number is represented in binary form in such a way that each gray-code number differs from preceding and that succeeding number by a single-bit. Gray code is non-weighted code it is more useful to use gray code than binary code.

Logic and Pin diagrams

i] Binary to Gray conversion

→ In this conversion the input straight binary number can easily be converted to its gray code equivalent.

1. Record the most significant bit as it is
2. Ex-OR this bit to the next position bit record the resultant bit
3. Record successive Ex-ORed bits until completed.
4. convert $(0101)_2$ to Gray.

Gray to Binary


$$C_{11011} \Rightarrow 100$$

$$\therefore B_2 = q_2$$

$$B_1 = B_2 \oplus q_1 = q_2 \oplus q_1$$

$$B_0 = B_1 \oplus q_0 = q_2 \oplus q_1 \oplus q_0$$

circuit diagram

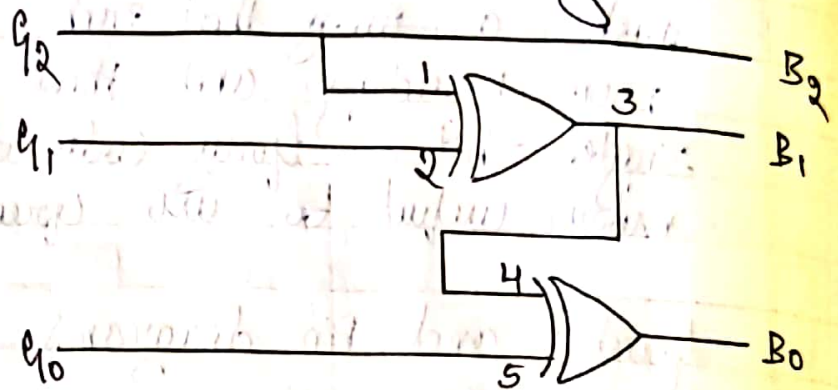

Gray code			Binary code		
q_2	q_1	q_0	B_2	B_1	B_0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	0
1	1	1	1	1	1

i] Gray to Binary Conversion:

1. The Gray code can be converted to binary by a simple process.
2. Record the most significant bit as it is
3. Ex-OR binary MSB to the next bit of Gray code and record the resultant bit
4. Continue the process until the LSB is recorded
5. Convert $(110)_2$ Gray to Binary.