

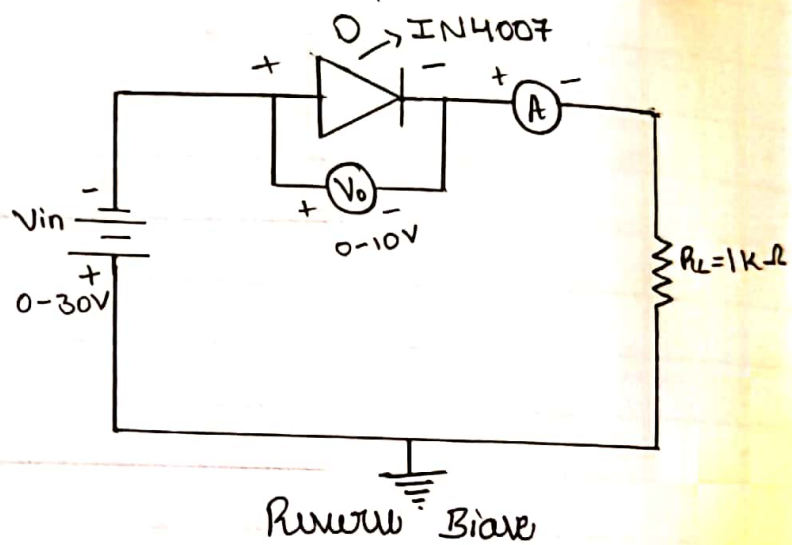


CIRCUIT DIAGRAM :

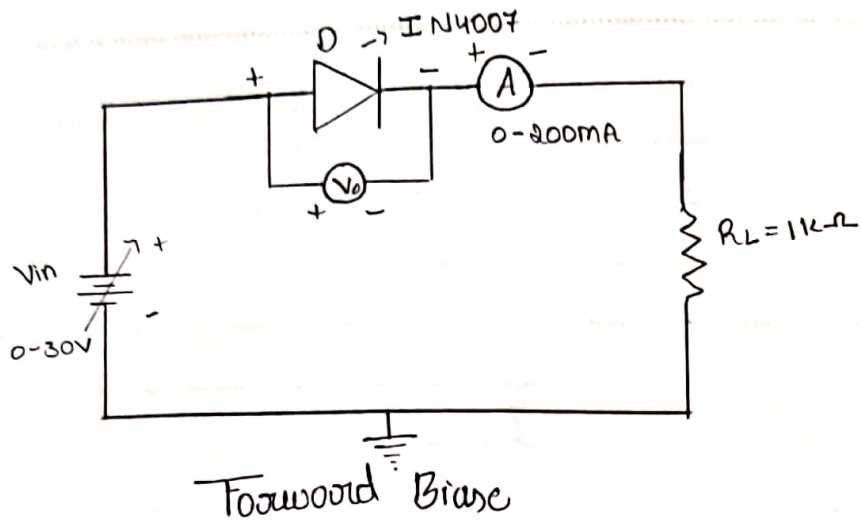

Expected waveform:

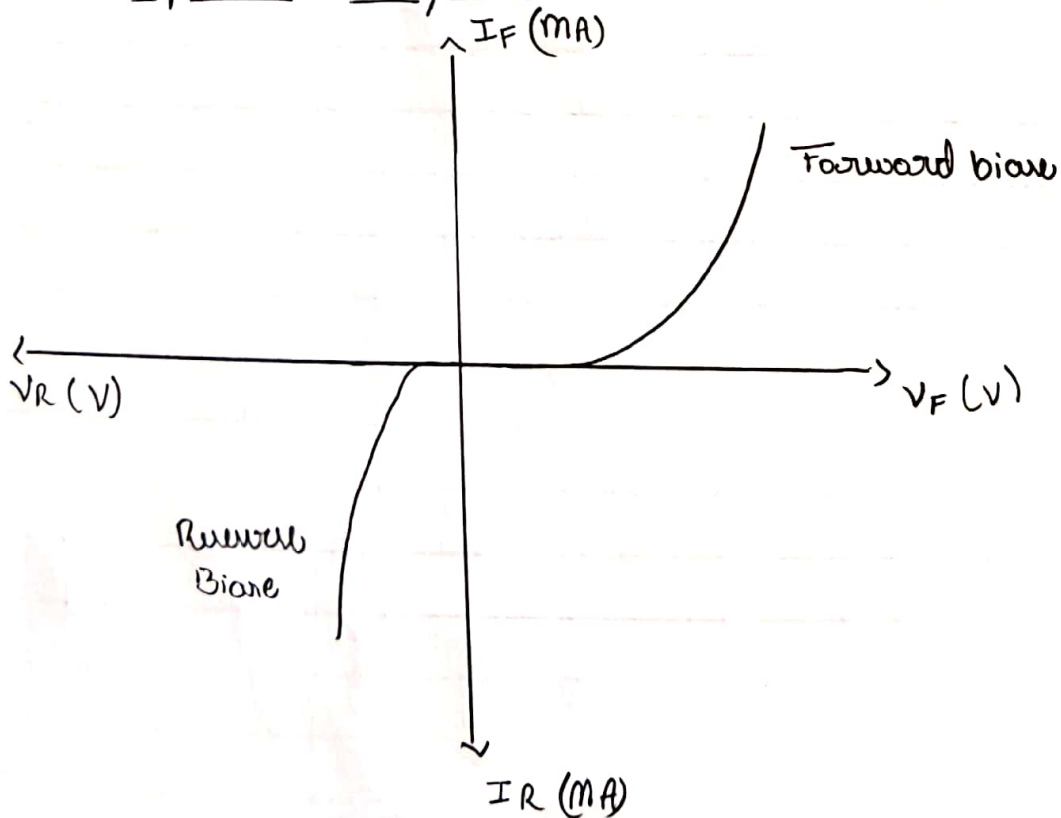

Name of the Experiment : V-I characteristics for P-N junction diode

Aim: To plot the V-I characteristics of P-N junction diode and Zener diode

APPARATUS REQUIRED:

- * Diode
- * Voltmeter
- * Ammeter
- * Resistor
- * Bread board
- * Connecting wires
- * DC-Power supply (0-30V) / Voltage source.

THEORY:

- * Diode is a semi-conductor device that essentially acts as a one-way switch for current in one direction flow.
- * If a single semi-conductor crystal is doped to P-type on one-side and n-type on the other, the area where the P and n-type region meet is called as P-N junction. The resulting device is a diode.
- * When P-n junction is formed some electron at the n-side are attracted and holes are on the P-side because of the ions accumulation, barrier voltage is created at the junction.

Tabular Column:

Forward bias:

V_{in}	V_R	I_R
0.2	0.2	0
0.4	0.4	0
0.6	0.5	0.1
0.8	0.5	0.2
1.0	0.6	0.4
2.0	0.6	0.5
3.0	0.6	2.5
4.0	0.6	3.6
5.0	0.6	4.6

Reverse bias:

V_{in}	V_R	I_R
0.0	0	0
0.2	-0.20	0
0.4	-0.39	0
0.6	-0.44	-0.2
0.8	-0.47	-0.4
1.0	-0.48	-0.6
2.0	-0.52	-1.6
3.0	-0.53	-2.7
4.0	-0.55	-3.7
5.0	-0.57	-4.8

* Diodes designed for operation in reverse breakdown are found its breakdown voltage that remains extremely stable over a wide of current levels. one such diode is termed as Zener Diode.

Result:

The $V-I$ characteristics for P-N junction diode and Zener diode is Plotted and verified.